




gEEK[®] spEEk

DC Block Capacitor Location (Does it matter?)

Presenter: Gustavo Blando

SCOPE

 


Where should we put Capacitors?

Close to TX or RX ?
Symmetry and Reciprocity
(S-parameters)
Time Domain Reflections



Test Cases

 Simple Capacitor Representation
Topologies
Some Math




Impedance Discontinuity in Capacitors

How to get a transparent
DC-Blocking cap?

Conclusions

SYMMETRY/RECIPROCITY

 

$$\begin{bmatrix} b1 \\ b2 \end{bmatrix} = \begin{bmatrix} S11 & S12 \\ S21 & S22 \end{bmatrix} \begin{bmatrix} a1 \\ a2 \end{bmatrix}$$

$$b1 = S11*a1 + S12*a2$$

$$b2 = S21*a1 + S22*a2$$


Symmetric → $S11 == S22$

Reciprocal → $S21 == S12$

 Most passive topologies
are **Reciprocal**, not **Symmetrical**



 


Figure 1: Simple topology, (capacitor close to one end)

 


WHO IS RIGHT?

 Let's look at Voltages
Measurement Points



 - For any given topology, same results are obtained, driving from left or right. (Fred was right!!)
- If we change the location of the capacitor, it's a different topology and results change (Tim is also sort of right!!)



LET'S COMPLICATE THINGS!!

Voltage Transfer Function

$$H(s) = \frac{V_2(s)}{V_s(s)} = \frac{S_{21}}{2} \left[\frac{(1 - \Gamma_S)(1 + \Gamma_L)}{(1 - S_{11}\Gamma_S)(1 - S_{22}\Gamma_L) - S_{12}S_{21}(\Gamma_S\Gamma_L)} \right]$$

Reflection Coefficient (source) & (load)



 
 


Figure 1: Simple topology, (capacitor close to one end)




 


REALLY? (LET'S LOOK AGAIN)

 

REFLECTIONS vs. POSITION

   
 
- How can we lower the reflections **simultaneously** at both ends?
- Let's do the following experiment:
 - Add Tx/Rx 200fF at the ends
 - Sweep location of DC-Blocking cap discontinuity
 - Compute ERL at side-1 and side-2 and power-sum**The bigger this number the less reflections $-20\log(V \text{ reflected})$**




SOLUTION IS SYSTEM DEPENDENT, BUT KEEP IN MIND THE TRENDS AND USE IT TO YOUR ADVANTAGE.

LET'S MINIMIZE DISCONTINUITIES

  
- Different ways to model DC-Blocking caps
- Important to reduce discontinuities




SHORT_VOID

 

COMPLEX_VOID

 

SIMPLE_VOID

 

TO CONCLUDE

- Same voltage transfer function, when driven from either side (+ Gain in unmatched cases)
- Reduce discontinuities by **simulating** your transitions
- Best capacitor location should be determined by understanding the **complete topology** including other discontinuities, (use losses to your advantage!!)



 
 


Figure 1: Simple topology, (capacitor close to one end)

 

REFERENCES

- **Signal Integrity Journal Article**
 - <https://www.signalintegrityjournal.com/authors/61-gustavo-j-blando>
- **DC-Blocking Cap Paper**
 - Designing DC-Blocking Capacitor Transitions to Enable 56Gbps NRZ & 112Gbps PAM4 (Scotty Neally, Scott McMorro, DesignCon 2018)
- **ERL Reference Material**
 - http://www.ieee802.org/3/cd/public/adhoc/archive/mellitz_080217_3cd_02_adhoc.pdf
 - <https://www.signalintegrityjournal.com/events/45-effective-return-loss-for-112g-and-56g-pam-4>
- **DFE Reference Material**
 - http://emlab.uiuc.edu/ece546/Lect_27.pdf

 

For information about Samtec's gEEK® spEEK presentations,
contact: gEEKspEEK@samtec.com

For Signal Integrity questions, contact: SIG@samtec.com

To view previous gEEK® spEEK webinar recordings,
go to www.samtec.com/geekspeek